

8

UTTARANCHAL UNIVERSITY, DEHRADUN
UTTARANCHAL SCHOOL OF COMPUTING SCIENCES
MID TERM EXAMINATION
EVEN SEMESTER 2023-24

BCA | 2nd Semester

FUNDAMENTAL OF COMPUTER ORGNAIZATION | BCA – C205

Time: 1:15 Hour

Max. Marks: 30

Note: All questions are compulsory.

Q.1- Answer the following questions.(1 x 6 = 6 Marks)

Multiple Choice Questions

- a) Which of the following operations is/are performed by the ALU?
(CO-5, BL-1)
- | | |
|----------------------|-----------------------|
| a. Data Manipulation | b. Exponential |
| c. Square Root | d. All of the above ✓ |
- b) Subtraction in computers is carried out by (CO-5, BL-1)
- | | |
|-------------------|---------------------|
| a. 1's complement | b. 2's complement ✓ |
| c. 3's complement | d. 9's complement ✓ |
- c) In which of the following form the computer stores its data in memory?(CO-3, BL-2)
- | | |
|---------------------|-----------------|
| a. Hexadecimal form | b. Octal form |
| c. Binary form ✓ | d. Decimal form |
- d) _____ are an example of the combinational circuit?(CO-3, BL-2)
- | | |
|--------------------|-------------------|
| a. Shift Registers | b. Multiplexers ✓ |
| c. Counters | d. Flip Flops |
- e) For which of the following gates the output is zero when one or more inputs are zero?(CO-3, BL-2)
- | | |
|--------|----------|
| a. OR | b. NOR |
| c. NOT | d. AND ✓ |
- f) Convert the binary equivalent 10101 to its decimal equivalent.
(CO-3, BL-2)
- | | |
|---------|-------|
| a. 21 ✓ | b. 12 |
| c. 22 ✓ | d. 31 |

725

Q.2-Write short note on any two (up to 70 words) (2 x 3 = 6 Marks)

- a) Explain AND and OR Gate with truth table and block diagram. (CO-2, BL-3)
- b) Explain the difference between Hardwired and Microprogrammed Control Units. (CO-3, BL-4)
- c) Solve $(6AC)_{16} = (?)_{10}$ (CO-2, BL-3)

Q.3-Attempt any one of the following (1 x 6 = 6 Marks)

- a) Explain 3X8 Decoder with a block diagram, truth table and logic diagram. (CO-2, BL-3)

OR

- b) Evaluate the Boolean function in SOP form and draw a logic diagram. (CO-3, BL-4)

$$F(A,B,C,D) = \sum m(4,5,7,12,14,15) + \sum d(3,8,10)$$

Q.4-Attempt any one of the following. (1 x 6 = 6 Marks)

- a) Explain Full Adder with a block diagram, truth table and logic diagram. (CO-4, BL-4)

OR

- b) Explain all types of Addressing Modes. CO-4, BL-4)

Q.5- Attempt any one of the following. (1 x 6 = 6 Marks)

- a) Explain Instruction Cycle with flow chart, and micro operations. (CO-4, BL-4)

OR

- b) Evaluate the Boolean function in SOP and POS form and draw a logic diagram. (CO-3BL4)

$$F(A,B,C,D) = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

Complement

8